

Digital Logic Design




Hajar Falahati

Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir

Encoder

  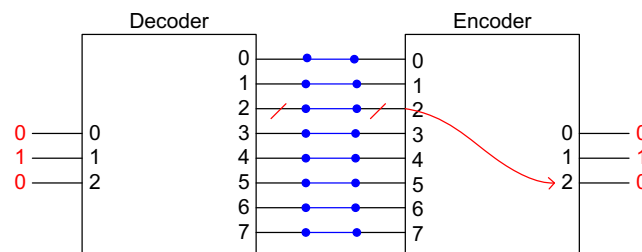- 2^n inputs and n outputs
- At each time **only one input** can be active
- **Generates the binary code corresponding to the input values**



Outline


- Multiplexer
- Demultiplexer



Multiplexer


Selecting

 - Suppose a logic has **more than one candidates** to its input
- Logic should **select** one of candidates
- **Which candidate does logic select as its input?**



Selection Logic

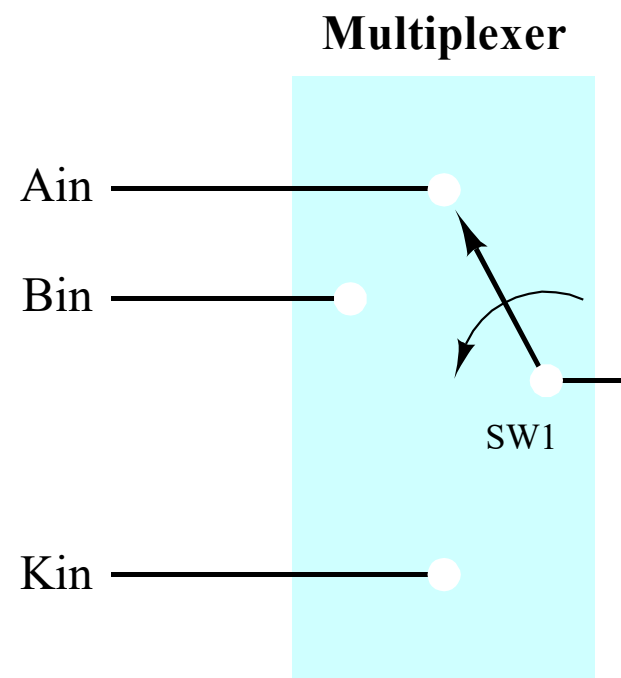- Characteristics of selection logic
 - A set of information inputs from which the selection is made
 - A set of control lines for making the selection
 - A single output
- Realization of selection logic
 - Multiplexer, a.k.a., MUX



Multiplexer

- Input



- n selection lines
- 2^n input lines

- Output

- 1 output line

- Function

 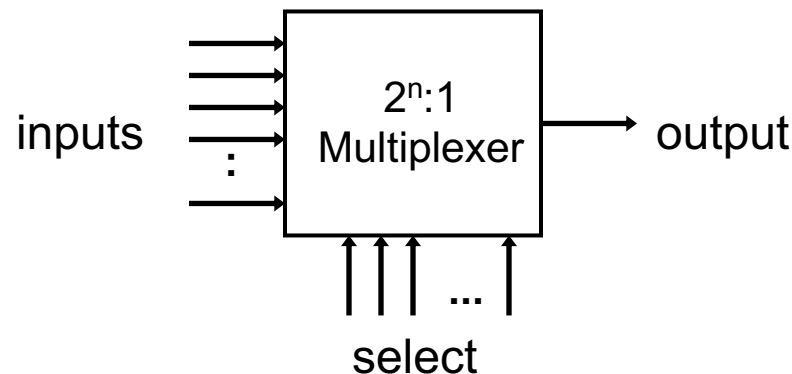- Uses **n selection lines**
- Selects **one** of 2^n inputs to a single output line



Multiplexer: 2-1

• Input



- 1 selection lines; S
- 2 input lines ; I_0 and I_1

• Output

- $S=0$; output = I_0
- $S=1$; output = I_1



S	Y
0	I_0
1	I_1

$$Y = \bar{S}I_0 + SI_1$$

  


Multiplexer 2-1: More Details

  - Three parts
 - 1-2 Decoder
 - 2 enabling circuits
 - 2-input OR gats
- 2×2 AND-OR circuit




Multiplexer: $2^n - 1$

 - Three parts
 - $n-2^n$ Decoder
 - $2^n \times 2$ AND-OR circuit




Multiplexer: 2^2-1

 - Three parts
 - $2-2^2$ Decoder
 - $2^2 \times 2$ AND-OR circuit




S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Multiplexer 2^2-1 : Realization

 


 Multiplexer 2^2-1 : Matrix Simplification




Expansion

 - Constructed from smaller MUXs
- Sample: Construct an 8-1 MUX




S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Expansion: 8-1 MUX

 


S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

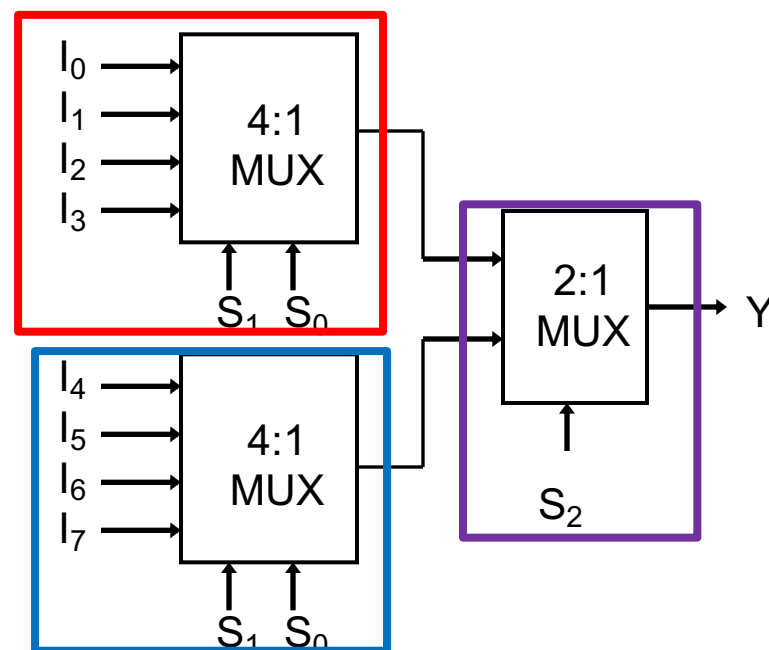

Sample 1


- Construct a 8-1 MUX using 2-1 MUX

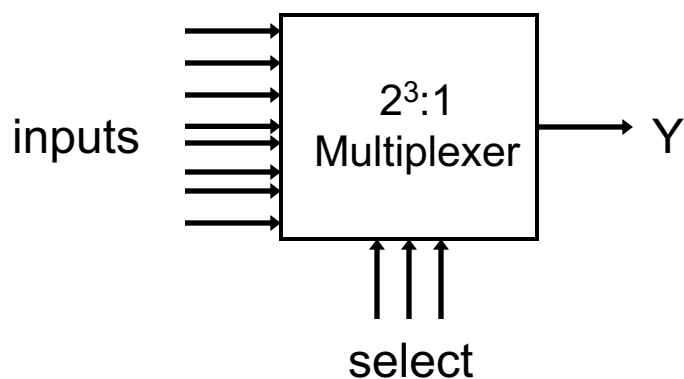

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Sample 1 (cont'd)

- Construct a 8-1 MUX using 2-1 MUX

 


S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Sample 1 (cont'd)

 


S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Sample 1 (cont'd)

 

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Sample 1 (cont'd)

 

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Sample 2

 - Construct a 8-1 MUX
 - 4 2-1 MUX
 - 1 4-1 MUX



S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Sample 2 (cont'd)

 

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Sample 3

- Construct a 16-1 MUX
 - 4-1 MUX

 

Sample 3 (cont'd)

- Construct a 16-1 MUX
 - 4-1 MUX


 


MUX & Universal Logic?

- Prove Mux is a UNIVERSAL logic



MUX Is a UNIVERSAL

- Implement **and** and **not**

 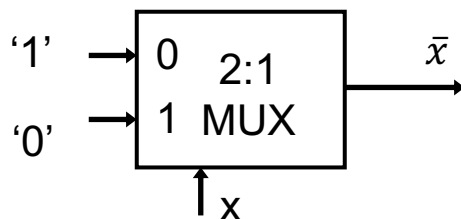


MUX Is a UNIVERSAL

- Implement **or** and **not**

  


Multiplexer: Chip

- 74151A
 - 8-1 MUX

 


(a)

 

Multiplexer: Chip (cont'd)

- 74151A
 - 8-1 MUX

 


Inputs				Outputs	
Select			Strobe $\overline{G}$	Y	W
C	B	A			
x	x	x	H	L	H
L	L	L	L	$\overline{D_0}$	$\overline{D_0}$
L	L	H	L	D_1	$\overline{D_1}$
L	H	L	L	D_2	$\overline{D_2}$
L	H	H	L	D_3	$\overline{D_3}$
H	L	L	L	D_4	$\overline{D_4}$
H	L	H	L	D_5	$\overline{D_5}$
H	H	L	L	D_6	$\overline{D_6}$
H	H	H	L	D_7	$\overline{D_7}$

(b)

Application

MUX Application

 Multiplexer/Demultiplexer Configuration of LinkBone switch



MUX Application

- Implement Boolean functions
- Inputs are **Product Terms (PT)**
- Selection lines are **variables**
- Steps
 - Present **SOP** form
 - Connect **n variables** to the **n selection lines**
 - Connect **input lines** to **'0'**
 - For each **PT**; connect corresponding input line to **'1'**

$$F = \sum_{i=0}^{i=n} m_i I_i$$

Sample 5


- Implement the function F using MUX
 - $F(A,B,C) = A'B'C + A'BC + AB'C + ABC'$

Sample 5: Realization

- Implement the function F using MUX

- $$F(A,B,C) = A'B'C + A'BC + AB'C + ABC'$$

$$F(A,B,C) = A'B'C + A'BC + AB'C + ABC' = \sum m(1,3,5,6)$$

 

Sample 6

- Implement the function F using 74151A MUX
 - $F(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$

Inputs				Outputs	
Select			Strobe		
C	B	A	$\bar{G}$	F	W
x	x	x	H	L	H
L	L	L	L	$\overline{D0}$	$\overline{D0}$
L	L	H	L	$D1$	$\overline{D1}$
L	H	L	L	$D2$	$\overline{D2}$
L	H	H	L	$D3$	$\overline{D3}$
H	L	L	L	$D4$	$\overline{D4}$
H	L	H	L	$D5$	$\overline{D5}$
H	H	L	L	$D6$	$\overline{D6}$
H	H	H	L	$D7$	$\overline{D7}$


Sample 6: Realization

- Implement the function F using 74151A MUX

- $$F(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$$

i	C	B	A	Y
	x_1	x_2	x_3	f
0	0	0	0	$1 D_0 = 1$
1	0	0	1	$0 D_1 = 0$
2	0	1	0	$1 D_2 = 1$
3	0	1	1	$1 D_3 = 1$
4	1	0	0	$0 D_4 = 0$
5	1	0	1	$1 D_5 = 1$
6	1	1	0	$0 D_6 = 0$
7	1	1	1	$0 D_7 = 0$

(a)

 

(b)

Sample 7

- Implement the function F using 4-1 MUX
 - $F(A,B,C) = A'B'C + A'BC + AB'C + ABC'$

Sample 7: Realization


- Implement the function F using 4-1 MUX

- $F(A,B,C) = \sum m(0,1,3,6)$
- $F(A,B,C) = A'B'C' + A'B'C + A'BC + ABC'$
- $= A'B' + A'B C + AB C'$
- $\Rightarrow AB = 00 \Rightarrow F(A,B,C) = 1$
- $\Rightarrow AB = 01 \Rightarrow F(A,B,C) = C$
- $\Rightarrow AB = 10 \Rightarrow F(A,B,C) = 0$
- $\Rightarrow AB = 11 \Rightarrow F(A,B,C) = C'$

Sample 7: Realization (cont'd)

- Implement the function F using 4-1 MUX

 - $F(A,B,C) = \sum m(0,1,3,6)$
- $F(A,B,C) = A'B'C' + A'B'C + A'BC + ABC'$
- $= A'B' + A'BC + ABC'$
- $\Rightarrow AB = 00 \Rightarrow F(A,B,C) = 1$
- $\Rightarrow AB = 01 \Rightarrow F(A,B,C) = C$
- $\Rightarrow AB = 10 \Rightarrow F(A,B,C) = 0$
- $\Rightarrow AB = 11 \Rightarrow F(A,B,C) = C'$



Realization with Smaller MUX


- Implement n variable function with $2^{n'}:1$ MUX; $n' = n - 1$
- Steps
 - Present **SOP** form
 - Connect **one variable** to the **input** line of MUX
 - Connect **other variables** to the **$n-1$ selection lines**
 - Draw the **truth table** for function
 - Grouping inputs by selection line values
 - Determine inputs

Sample 8

- Implement the function F using 4-1 MUX
- Consider A as input line
 - $F(A,B,C) = \sum m(0,1,3,6)$

Sample 8: Realization

- $F(A,B,C) = \sum m(0,1,3,6)$
 - $F(A,B,C) = A'B'C' + A'B'C + A'BC + ABC'$
 - $= B'C' (A') + B'C (A') + BC' (A) + BC(A')$
 - $\Rightarrow BC = 00 \Rightarrow F(A,B,C) = A'$
 - $\Rightarrow BC = 01 \Rightarrow F(A,B,C) = A'$
 - $\Rightarrow BC = 10 \Rightarrow F(A,B,C) = A$
 - $\Rightarrow BC = 11 \Rightarrow F(A,B,C) = A'$

 

Sample 9

- Implement the function F using 74151A MUX (8-1 MUX)
- $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 3, 4, 9, 13, 14, 15)$


Inputs				Outputs	
Select			Strobe		
C	B	A	$\bar{G}$	Y	W
x	x	x	H	L	1
L	L	L	L	D0	$\bar{D0}$
L	L	H	L	D1	$\bar{D1}$
L	H	L	L	D2	$\bar{D2}$
L	H	H	L	D3	$\bar{D3}$
H	L	L	L	D4	$\bar{D4}$
H	L	H	L	D5	$\bar{D5}$
H	H	L	L	D6	$\bar{D6}$
H	H	H	L	D7	$\bar{D7}$

(b)

Sample 9: Realization

- Implement the function F using 74151A MUX (8-1 MUX)
- $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 3, 4, 9, 13, 14, 15)$


	C	B	A				Y
i	X_1	X_2	X_3	X_4	f	f	
0	0	0	0	0	1		
	0	0	0	1	1	1	$D_0 = 1$
1	0	0	1	0	1		
	0	0	1	1	1	1	$D_1 = 1$
2	0	1	0	0	1		
	0	1	0	1	0	$\bar{X}_4$	$D_2 = \bar{X}_4$
3	0	1	1	0	0		
	0	1	1	1	0	0	$D_3 = 0$
4	1	0	0	0	0		
	1	0	0	1	1	X_4	$D_4 = X_4$
5	1	0	1	0	0		
	1	0	1	1	0	0	$D_5 = 0$
6	1	1	0	0	0		
	1	1	0	1	1	X_4	$D_6 = X_4$
7	1	1	1	0	1		
	1	1	1	1	1	1	$D_7 = 1$

 

Demultiplexer


Demultiplexing

 - Suppose a logic has **one input data** and **some candidates** on its **output**
- Logic should **select** one of candidates
- **Selection logic**
 - Select output line
 - Send data to the selected output line





Demultiplexer

- Input
 - n selection lines
 - 1 input line
- Output
 - 2^n output lines
- Function
 - Uses **n selection** lines
 - Selects **one** of 2^n outputs

 

Multiplexer VS. Demultiplexer

  


Demultiplexer: 1-4

- Input

- 2 selection lines
- 1 input line

- Output

- 2^2 output lines

 


Demultiplexer: 1-4 (cont'd)

- **Input**

- 2 selection lines
- 1 input line


- **Output**

- 2^2 output lines

 

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

Demultiplexer: 1-4 (cont'd)

 


S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

Demultiplexer Vs. Decoder

Demultiplexer = An Enabled Decoder

 - A decoder with **enable** signal
- Inputs
 - Selection lines of demultiplexer
- **Enable Input**
 - Input line of demultiplexer
- **Output**
 - 2^2 output lines of demultiplexer



Thank You

